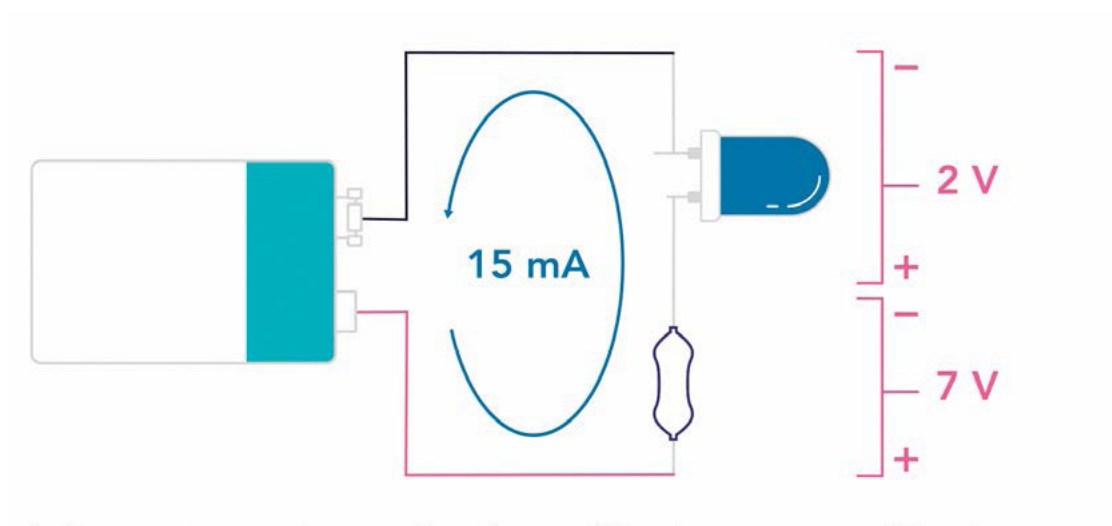


Challenge

Challenge: Choose the resistance value to limit current

LED Characteristics

- Very little resistance—pretend “0 Ω ”
- Target current = 15 mA
- Voltage drop = 2 V



Goal: Determine resistor value that will limit current to 15mA