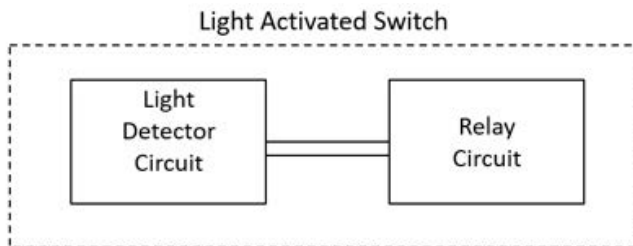


Challenge



Challenge: Design the light detector circuit for a light-activated switch.



Circuit Description

The light detector circuit is built using a Wheatstone bridge to produce a differential output voltage.

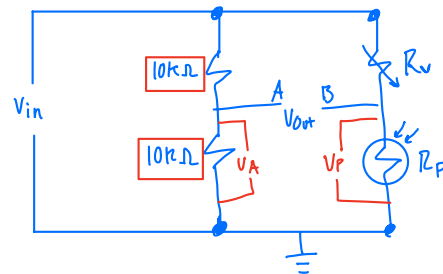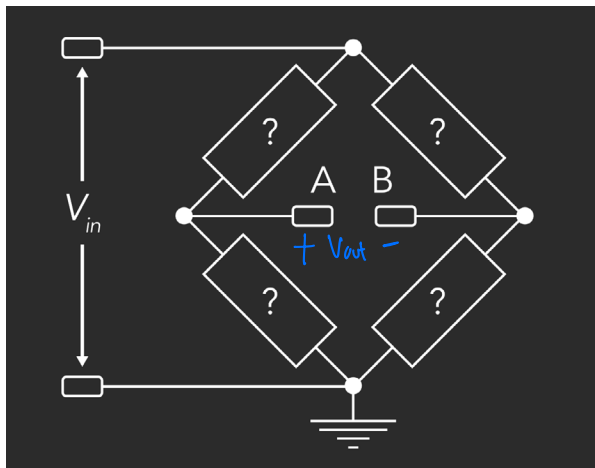- When the circuit is under light, Voltage A should be greater than Voltage B.
- When the circuit is in the dark, Voltage B should be less than or equal to Voltage A.



$$V_A = V_{in} \frac{10k\Omega}{10k\Omega + 10k\Omega}$$

$$V_{in} = 5V$$

$$V_A = 2.5V$$

Set $R_p = R_v$ so $V_A = V_p$ at the calibration light level

$R_p = R_v = 5k\Omega$ at light level

Goal: Determine the value and location of the following components within the Wheatstone bridge.

- Photoresistor (approximately $1k\Omega$ in the light/ $10k\Omega$ in the dark)
- Variable resistor
- Constant-value resistors