

Challenge

Challenge: Design a passive RC filter.

Filter Requirements

- Attenuate frequencies above $f_{-3dB} \approx 150$ Hz.
- A 3dB cutoff frequency of $f_c =$ of $150 \text{ Hz} \pm 10 \text{ Hz}$ is “close enough.”

Goal: Choose a combination of resistors and capacitors that meet the filter requirements.