

Challenge

Challenge: Design a passive RC filter.

Filter Requirements

- Attenuate frequencies above $f_{-3dB} \approx 150$ Hz.
- A 3dB cutoff frequency of f_c = of $150 \text{ Hz} \pm 10 \text{ Hz}$ is “close enough.”

Goal: Choose a combination of resistors and capacitors that meet the filter requirements.



$$f_c = 150 \text{ Hz} = \frac{1}{2\pi \cdot R \cdot C} \Rightarrow C = \frac{1}{2\pi \cdot 10,000 \cdot 150} = 106 \text{ nF} \Rightarrow 100 \text{ nF}$$

$$R = 10 \text{ k}\Omega$$

$$C = 100 \text{ nF}$$

$$f_c = \frac{1}{2\pi \cdot 10 \text{ k}\Omega \cdot 100 \text{ nF}} = 159 \text{ Hz}$$