


Low-Pass RC Filter Circuit

This circuit is a simple low-pass RC filter with a cutoff frequency of 1,592 Hz.

Components

- 10 k Ω resistor
- 10 nF capacitor

Schematic

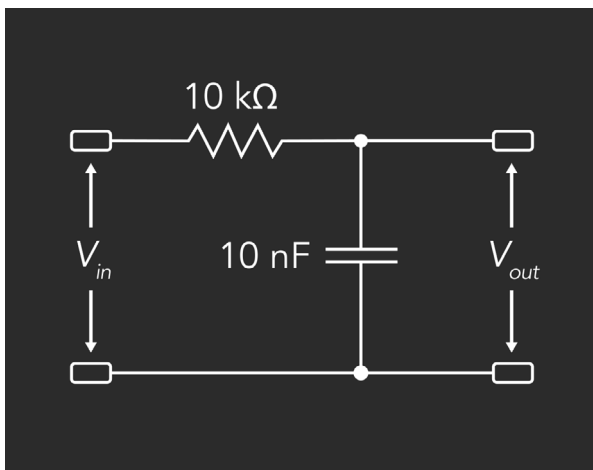

Circuit

