


RL Circuit

This circuit demonstrates how the voltage across an inductor changes when a voltage is applied to an RL circuit.

Components

- 5 V power source
- Switch
- $100\ \Omega$ resistor
- $100\ \mu\text{H}$ inductor

Schematic

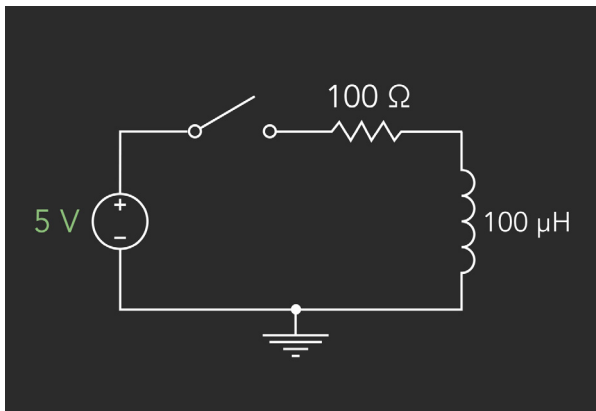

Circuit

