


Parallel Resistor Circuit

This circuit was used to demonstrate the result of combining resistors in parallel.

Components

- 10 k Ω resistor
- 20 k Ω resistor (use two 10 k Ω resistors in series)

Schematic

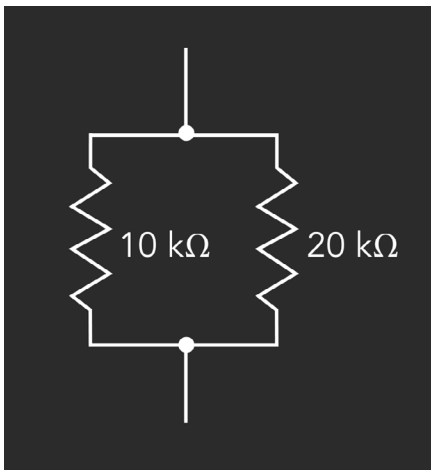

Circuit

